

# Time Constants for an RC Circuit and an LR Circuit

Ryan Coyne

May 2, 2023

## 1 Abstract/Procedure/Conclusion

In this lab, we measured the time constants,  $\tau$ , for three RC and three LR circuits. Each RC circuit was set up as in Figure 1. The first had a resistor with a resistance of  $100\ \Omega$  and a capacitor with a capacitance of  $330\ \mu\text{F}$ . The second had a resistor with a resistance of  $10\ \Omega$  and a capacitor with a capacitance of  $100\ \mu\text{F}$ . The first had a resistor with a resistance of  $10\ \Omega$  and a capacitor with a capacitance of  $100\ \mu\text{F}$ . The LR circuits were set up as shown in Figure 2. They all used the same inductor with an inductance of  $8.2\ \text{mH}$  and a resistance of  $6.5\ \Omega$ . The first had a resistor with a resistance of  $10\ \Omega$ . The second had a resistor with a resistance of  $33\ \Omega$ . The third had a resistor with a resistance of  $100\ \Omega$ . The power source was a signal generator set to create a square wave with a frequency around  $1\ \text{kHz}$  and an amplitude of  $5\ \text{V}$ .

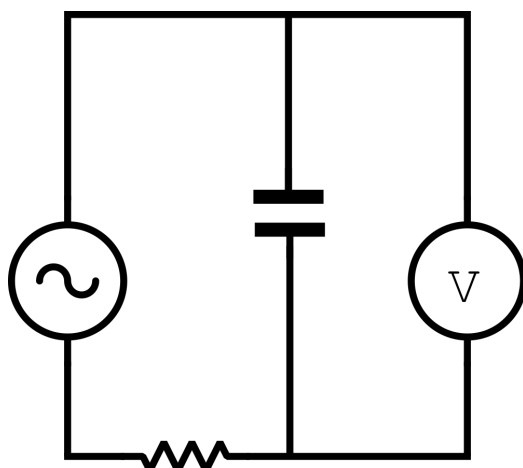


Figure 1: RC circuit: Experimental setup

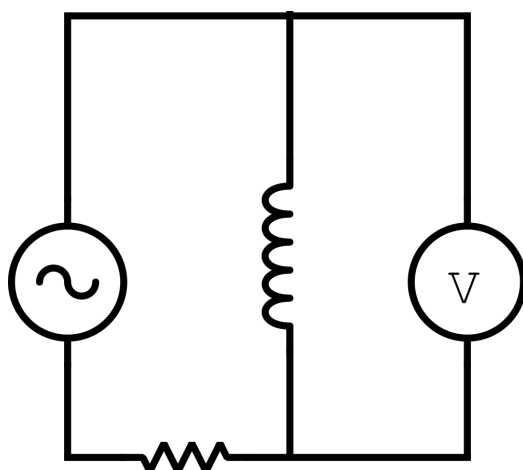


Figure 2: LR circuit: Experimental setup

## 2 Data

	$C$ ( $\mu\text{F}$ )	$R$ ( $\Omega$ )	$\tau$ (s)	$\tau_{meas}$ (s)
1	330	100	0.033	0.036
2	100	10	0.0010	0.0011
3	100	33	0.0033	0.0036

Table 1: RC circuit: Capacitance and resistance.

	$L$ (H)	$R$ ( $\Omega$ )	$\tau$ (s)	$\tau_{meas}$ (s)
1	0.0082	16.5	0.000497	0.000078
2	0.0082	39.5	0.00021	0.00021
3	0.0082	106.5	0.000077	0.00051

Table 2: LR circuit: Inductance and resistance.

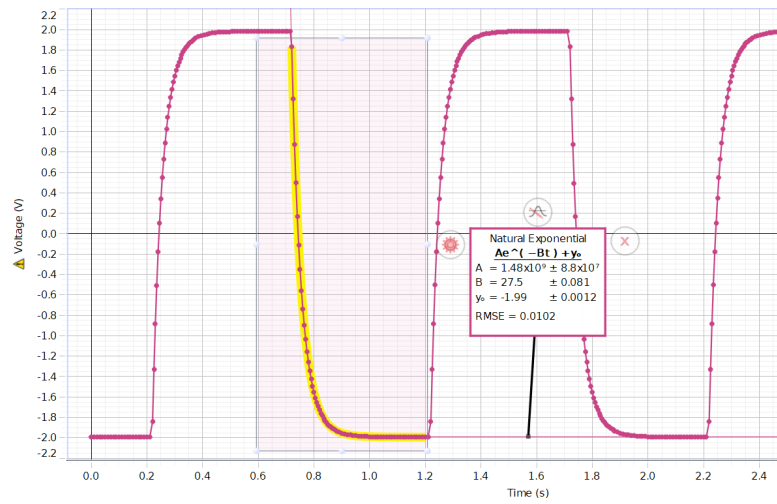


Figure 3: RC circuit 1 plot.

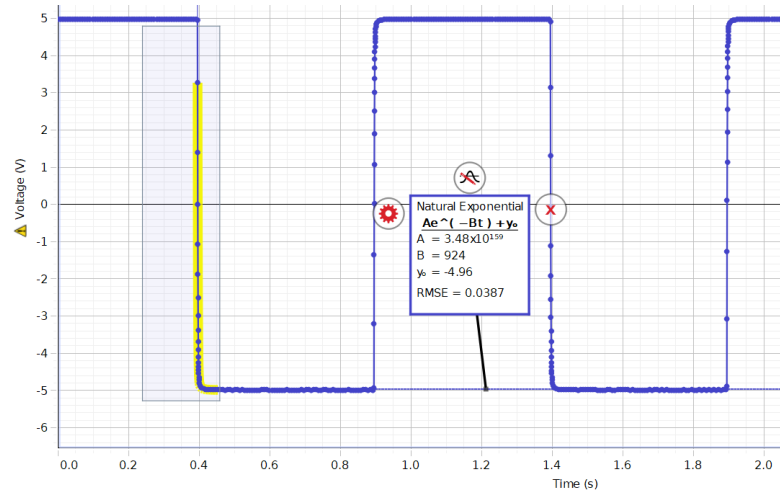


Figure 4: RC circuit 2 plot.

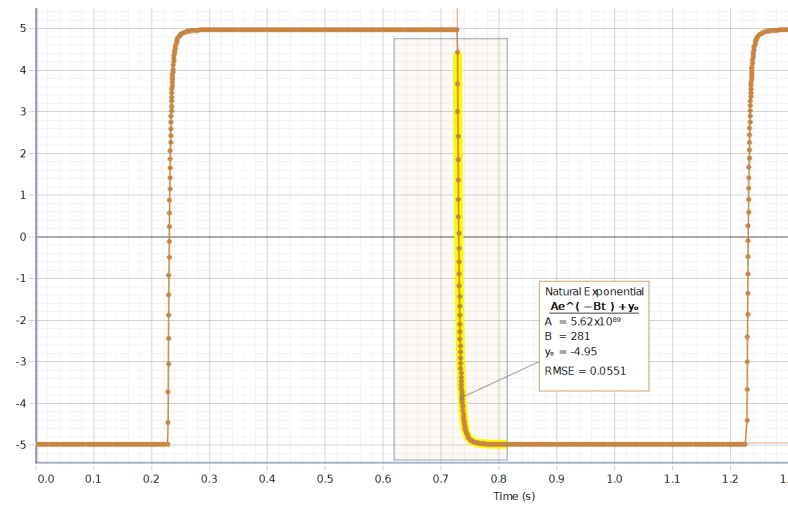


Figure 5: RC circuit 3 plot.

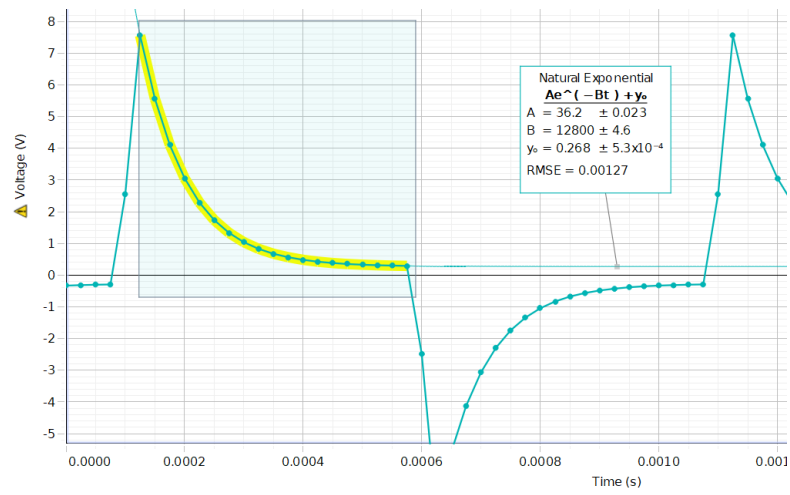


Figure 6: LR circuit 1 plot.

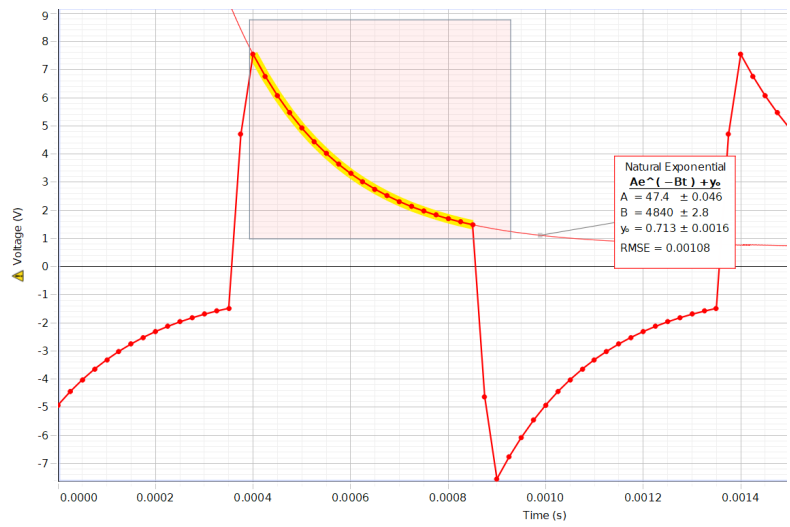


Figure 7: LR circuit 2 plot.

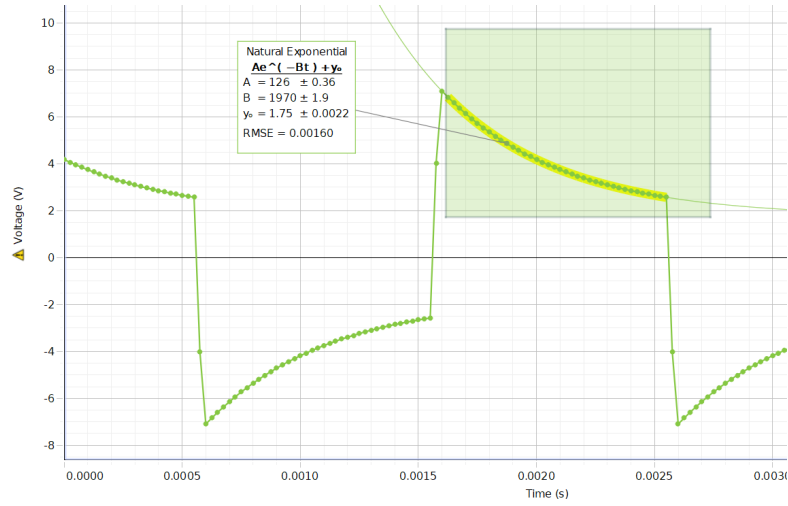


Figure 8: LR circuit 3 plot.

### 3 Calculations

$$(1) \quad Q = C\Delta V_c$$

$$(2) \quad \sigma_{R_1} = 5 \, \Omega$$

$$\sigma_{R_2} = 1.65 \, \Omega$$

$$\sigma_{R_3} = 0.5 \, \Omega$$

$$\frac{\sigma_{R_1}}{R_1} = \frac{5 \, \Omega}{100 \, \Omega}$$

$$\frac{\sigma_{R_2}}{R_2} = \frac{1.65 \, \Omega}{33 \, \Omega}$$

$$\frac{\sigma_{R_3}}{R_3} = \frac{0.5 \, \Omega}{10 \, \Omega}$$

$$\frac{\sigma_{R_1}}{R_1} = \frac{\sigma_{R_2}}{R_2} = \frac{\sigma_{R_3}}{R_3}$$

$$= 5\%$$

$$\sigma_{C_1} = 66 \, \mu\text{F}$$

$$\sigma_{C_2} = 20 \, \mu\text{F}$$

$$\frac{\sigma_{C_1}}{C_1} = \frac{66 \, \mu\text{F}}{330 \, \mu\text{F}}$$

$$\begin{aligned}
\frac{\sigma_{C_2}}{C_2} &= \frac{20 \mu\text{F}}{100 \mu\text{F}} \\
\frac{\sigma_{C_1}}{C_1} &= \frac{\sigma_{C_2}}{C_2} \\
&= 20\% \\
(3) \quad \overline{\tau}_1 &= 330 \mu\text{F} \cdot 100 \Omega \\
&= 0.033 \text{ s} \\
\tau_{1,R} &= 330 \mu\text{F} \cdot (100 + 5) \Omega \\
&= 0.03465 \text{ s} \\
\tau_{1,C} &= (330 + 66) \mu\text{F} \cdot 100 \Omega \\
&= 0.0396 \text{ s} \\
\sigma_{\tau_1} &= 0.0068 \text{ s} \\
(4) \quad \sigma_{R_4} &= 0.825 \Omega \\
\sigma_{R_5} &= 1.975 \Omega \\
\sigma_{R_6} &= 5.325 \Omega \\
\frac{\sigma_{R_4}}{R_4} &= \frac{0.825 \Omega}{16.5 \Omega} \\
\frac{\sigma_{R_5}}{R_5} &= \frac{1.975 \Omega}{39.5 \Omega} \\
\frac{\sigma_{R_6}}{R_6} &= \frac{5.325 \Omega}{106.5 \Omega} \\
\frac{\sigma_{R_4}}{R_4} &= \frac{\sigma_{R_5}}{R_5} = \frac{\sigma_{R_6}}{R_6} \\
&= 5\% \\
(5) \quad \overline{\tau}_4 &= \frac{0.0082 \text{ H}}{16.5 \Omega} \\
&= 0.000497 \text{ s} \\
\tau_{4,R} &= \frac{0.0082 \text{ H}}{(16.5 + 0.825) \Omega} \\
&= 0.000473 \text{ s} \\
\sigma_{\tau_4} &= \overline{\tau}_4 - \tau_{4,R} \\
&= 0.000497 \text{ s} - 0.000473 \text{ s} \\
&= 0.000024 \text{ s}
\end{aligned}$$